

Ejercicio

$$f : \{0, 1\} \rightarrow \{0, 1\}$$

constantes

equilibradas

$$f_0 \begin{cases} 0 \mapsto 0 \\ 1 \mapsto 0 \end{cases}$$

$$f_2 \begin{cases} 0 \mapsto 0 \\ 1 \mapsto 1 \end{cases}$$

$$f_1 \begin{cases} 0 \mapsto 1 \\ 1 \mapsto 1 \end{cases}$$

$$f_3 \begin{cases} 0 \mapsto 1 \\ 1 \mapsto 0 \end{cases}$$

Escribir los circuitos y las matrices de los oráculos O_{f_0} , O_{f_1} , O_{f_2} y O_{f_3}

Oráculo para f

$$\begin{array}{l} |x\rangle \\ |y\rangle \end{array} \begin{array}{c} \boxed{O_f} \\ \end{array} \begin{array}{l} |x\rangle \\ |y \oplus f(x)\rangle \end{array} \quad \begin{array}{l} x \in \{0, 1\}^n \quad y \in \{0, 1\} \\ O_f \text{ permuta vectores de la base} \end{array}$$


$$0 \oplus 0 = 0 \quad 1 \oplus 0 = 1 \quad 0 \oplus 1 = 1 \quad 1 \oplus 1 = 0 \quad [\oplus : \text{XOR}]$$

$$O_f |x, y\rangle = |x, y \oplus f(x)\rangle \quad [\text{Notación: } |x\rangle \otimes |y\rangle = |x\rangle |y\rangle = |x, y\rangle = |xy\rangle]$$

$$O_f O_f |x, y\rangle = O_f |x, y \oplus f(x)\rangle = |x, y \oplus f(x) \oplus f(x)\rangle = |x, y \oplus 0\rangle = |x, y\rangle$$

$$O_f = O_f^{-1} \quad O_f \text{ es hermitiano (unitario y autoinversa)}$$


$$f_0(0) = 0 \quad f_0(1) = 0$$

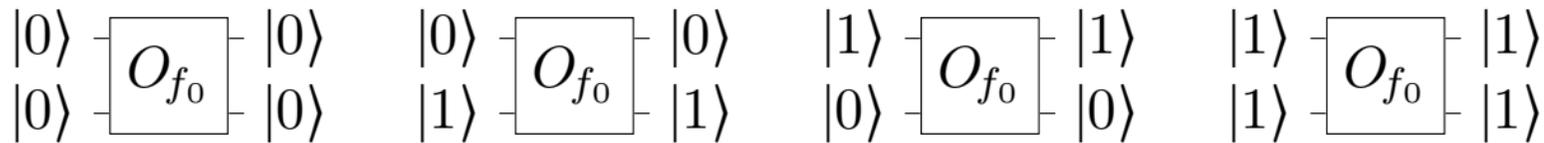

$$O_{f_0} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$


el circuito es:

$$f_1(0) = 1 \quad f_1(1) = 1$$

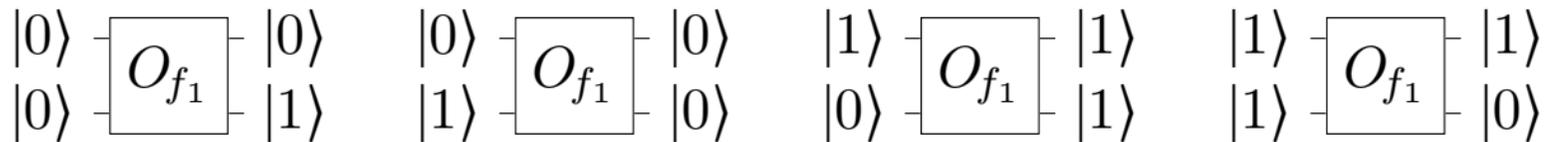


$$O_{f_1} = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

el circuito es:

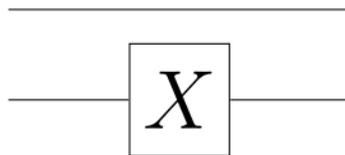


$$f_2(0) = 0 \quad f_2(1) = 1$$

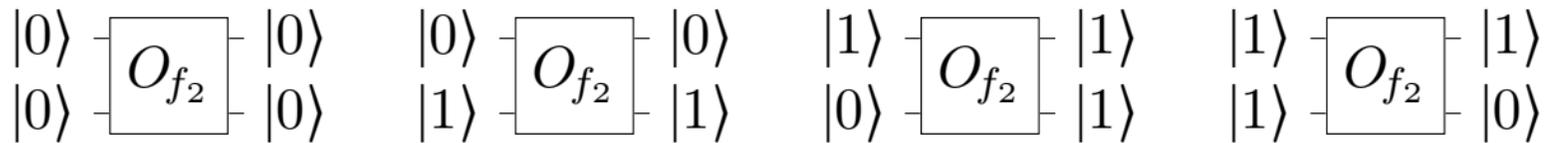

$$O_{f_2} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

el circuito es:

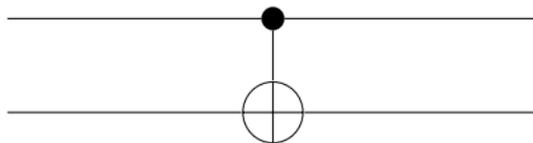

Ejemplo con f_3

$$f_3(0) = 1 \quad f_3(1) = 0$$

[f_3 : NOT]

$$\begin{array}{c} |0\rangle \\ |0\rangle \end{array} \begin{array}{c} \boxed{O_{f_3}} \\ \end{array} \begin{array}{c} |0\rangle \\ |1\rangle \end{array}$$

$$\begin{array}{c} |0\rangle \\ |1\rangle \end{array} \begin{array}{c} \boxed{O_{f_3}} \\ \end{array} \begin{array}{c} |0\rangle \\ |0\rangle \end{array}$$

$$\begin{array}{c} |1\rangle \\ |0\rangle \end{array} \begin{array}{c} \boxed{O_{f_3}} \\ \end{array} \begin{array}{c} |1\rangle \\ |0\rangle \end{array}$$

$$\begin{array}{c} |1\rangle \\ |1\rangle \end{array} \begin{array}{c} \boxed{O_{f_3}} \\ \end{array} \begin{array}{c} |1\rangle \\ |1\rangle \end{array}$$

$$O_{f_3} |00\rangle = \begin{pmatrix} 0 \\ 1 \\ 0 \\ 0 \end{pmatrix}$$

$$O_{f_3} |01\rangle = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$O_{f_3} |10\rangle = \begin{pmatrix} 0 \\ 0 \\ 1 \\ 0 \end{pmatrix}$$

$$O_{f_3} |11\rangle = \begin{pmatrix} 0 \\ 0 \\ 0 \\ 1 \end{pmatrix}$$

$$O_{f_3} = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$

$$O_{f_3} \begin{pmatrix} \alpha \\ \beta \\ \gamma \\ \delta \end{pmatrix} = \begin{pmatrix} \beta \\ \alpha \\ \gamma \\ \delta \end{pmatrix}$$

el circuito para f_3 es:

